 


VERILOG-BASICS

How to write a basic Verilog code and test bench?
-Language constructs

Basic building blocks: modules

- A design in Verilog is modeled using the concept of “**module**”.
- A module will have two parts
 - A port declaration part
 - A functional description part
- Module declarations cannot be nested.
- Modules are:
 - Declared
 - Instantiated
- A module may contain any of the following items:
 - *data_type_declarations*
 - *parameter_declarations*
 - *module_instances*
 - *primitive_instances*
 - *generate_blocks*
 - *procedural_blocks*
 - *continuous_assignments*
 - *task_definitions*
 - *function_definitions*
 - *specify_blocks*



ANSI C style
port list

```
module buffer (output Z, input in);  
    assign #1 Z = in;  
endmodule
```

Old style
port list

```
module buffer (Z, in);  
    output Z;  
    input in;  
    assign #1 Z = in;  
endmodule
```

Ports and Comments


- Module interface is defined using **ports**. Each port must be explicitly declared as one of the following types:
 - *input*
 - *output*
 - *inout*
- Ports can be
 - *Scalar (single bit) - don't specify a size*
input cin;
 - *Vector (multiple bits) - specify size using range*
Range is MSB to LSB (left to right)
Don't have to include zero (D[2:1])
output [7:0] OUT;
input [0:4] IN;
- Verilog supports 2 type of **comment** syntaxes
 - *Single line comment start with //, and end with newline.*
 - *Block comment, start with /*, and end with */. Block comment cannot be nested.*
- Example
 - /* This is how you comment out a number of lines in Verilog. Can be used to intricately describe a code. The comment stops where it encounters this => */*
input status; // 0:ready, 1:not ready
output data; // sync with clock mClock

Levels of Modeling

- Structural
 - *Use primitives and lower-level module instantiations.*
 - *Logic gates and Verilog primitives*
 - *Very close to physical implementation.*
 - *Easy (straightforward) synthesis.*
- Dataflow
 - *Define output signals in terms of input signal transformations.*
- Behavioral
 - *Specify algorithmically the expected behavior of the system.*
 - *Close to natural language description.*
 - *Most difficult to synthesize.*
 - *Best for verification.*

Structural Modeling

- Structural elements of a Verilog structural description are logic gates and user-defined components connected by wires
- Structural description can be viewed as a simple netlist composed of nets that connect instantiations of gates.
- Primitives are pre-defined gates already described in the Verilog language.
- Advantages:
 - *Hand-Designed systems always the most efficient*
 - *Power, area, frequency requirement can be most accurately met by designer.*
 - *Existence of proven sub-blocks*
 - *IP-Cores readily available*
- Disadvantages
 - *This kind of modeling can get tedious for very large designs*
 - *Architecture / hardware of problem being solved may not be known always*
 - *Arriving at structure first and then modeling it will take lots of time*
 - *Building edge triggered circuits with structural modeling alone can be very tricky*
- Though being ideally the best way to model a hardware time-to-market issues and complexity involved works against it.

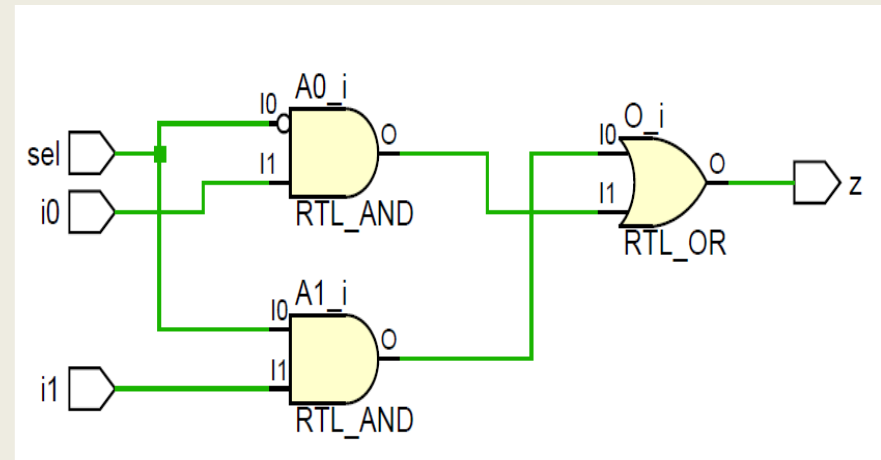

```
//2-to-1 Multiplexer
module mux2(
    output z,
    input i0, i1, sel );
    wire nsel,a0,a1;
    not inv (nsel, sel);
    and A0(a0, nsel, i0);
    and A1(a1,sel,i1);
    or O(z,a1,a0);
endmodule
```

Using primitives

- Pre-defined gates already described in the Verilog language
- Can have only one output but any number of inputs. They need not be declared, they are only called.
- First variable in port list of primitive is always output and naming of primitives is optional.
- Language has no restriction on inputs but depends on technology being targeted to.
- Delays can be specified again optionally.
- Any number of gates of same functionality can be called in single line.
- Basic combinational gates are available as primitives.
- Used directly in the code as smaller case key-words.
- Some examples :and, nand, or, nor, not, xor, xnor.

```
//1-bit Adder
module adder(
    output sum, carry,
    input a, b, cin);
    xor XO (sum,a,b,cin);
    and A0(a0, a,b),
        A1(a1,b,cin),
        A2(a2,cin,a);
    or O(carry,a0,a1,a2);
endmodule
```

Component Instantiation

- Instantiation
 - *Predefined modules can be called just like primitives*
 - *An Instance is a unique copy of a pre-defined module.*
 - *Predefined modules are connected to one another by means of nets.*
- Component instantiation can be done in two ways
 - *Named port connection / calling by reference.*
 - *Ordered port connection / calling by position.*
- Most simulators /synthesis tools require components to be compulsory named
- Component instantiations do not accommodate delays like primitives.
- While simulating component should have been compiled before it can be called in a top module.

```
// 4-to-1 multiplexer
module mux4(
  input d0,d1,d2,d3,
  input [1:0] sel,
  output z);
  wire z1,z2;
  /*instances must have unique names within
  current module. Connections are made using
  .portname(expression) syntax.*/
  // order doesn't matter...
  mux2 m1(.sel(sel[0]),.i0(d0),.i1(d1),.z(z1));
  mux2 m2(.sel(sel[0]),.i0(d2),.i1(d3),.z(z2));
  mux2 m3(.sel(sel[1]),.i0(z1),.i1(z2),.z(z));
  /*could also write "mux2 m3(z,z1,z2,sel[1])"
  NOT A GOOD IDEA! */
endmodule
```

Dataflow Modeling

- Dataflow modeling consists of **continuous assignment statements**
 - They start with the keyword *'assign'*. These statements are always active.
 - They are executed whenever there is a change in a variable on the right hand side of the statement.
 - They are used when the system being designed can be completely represented in Boolean equation format.
 - Several assignment statements are concurrent in nature(they execute in parallel).
 - They can also represent the propagation delay from input to output.
- This type of execution model is called “**dataflow**” since evaluations are triggered by data values flowing through the network of **wires** and **operators**.

```
// 2-to-1 multiplexer with dual-polarity outputs  
module mux2(  
  input i0,i1,sel,  
  output z,zbar);  
// again order doesn't matter (concurrent execution!)  
// syntax is "assign LHS = RHS" where LHS is a wire/bus  
// and RHS is an expression  
  assign z = sel ? i1 : i0;  
  assign zbar = ~z;  
endmodule
```


Vectors and Parameters

■ Parameters are run time constants

- Are declared within a module
- Their scope lies within the module
- Can be overwritten during component instantiation
- Used to make a code scalable
- Module can have more than one parameter

// 2-to-1 multiplexer, W-bit data

```
module mux2 #(parameter W=1) // data width, default 1 bit
( input [W-1:0] i0,i1,
  input sel,
  output [W-1:0] z );
  assign z = sel ? i1 : i0;
endmodule
```

■ Signals which are multi-bits are declared as vectors

- Can be declared as [high:low] or [low:high]
- Common usage is **[MSB:LSB]** where $MSB > LSB$; usually LSB is 0.
- A bit of the vector is accessible.
- Examples:

```
wire [n:0] carry_wires // vector being declared
carry_wires[5:2] = 4'd1010 // part of vector being
                           //assigned value
outp = carry_wires[5:3] // part of vector being
                       //accessed
```

// 4-to-1 multiplexer, W-bit data

```
module mux4 #(parameter W=2) // data width, default 2 bit
( input [W-1:0] d0,d1,d2,d3,
  input [1:0] sel,
  output [W-1:0] z);
  wire [W-1:0] z1,z2;
  mux2 #(.W(W)) m1(.sel(sel[0]),.i0(d0),.i1(d1),.z(z1));
  mux2 #(.W(W)) m2(.sel(sel[0]),.i0(d2),.i1(d3),.z(z2));
  mux2 #(.W(W)) m3(.sel(sel[1]),.i0(z1),.i1(z2),.z(z));
endmodule
```

Language conventions and semantics

Conventions:

- Verilog is case-sensitive
- Some simulators are case-insensitive
- Advice: - Don't use case-sensitive feature!
- Keywords are always lower case
- Different names must be used for different items within the same scope
- Identifiers can have
 - ✓ *Upper case and lower case alphabets*
 - ✓ *Decimal Digits (but should not start with digits)*
 - ✓ *Underscore (again not at the beginning)*

Semantics:

- All statements are terminated with ';'
- Comments :
 - ✓ *all characters after '//' in a line are treated as comments*
 - ✓ *multiple line comments begin and end with '*'*
- Compiler directives begin with `
- Built in system task and functions begin with '\$'
- Strings enclosed with double quotes must be on one line

Four valued logic

Since we're describing hardware, we'll need to represent the values that can appear on wires. Verilog uses a 4-valued logic. A single bit can have one of FOUR values:

- ❑ "0" → Numeric 0, logical FALSE, "low"
- ❑ "1" → Numeric 1, logical TRUE, "high"
- ❑ "x" → Unknown or ambiguous value
- ❑ "z" → No value (high impedance)

Why x?

– Could be a conflict, could be lack of initialization

Why z?

– Nothing driving the signal, Tri-states

Verilog also has the notion of "drive strength" but we can safely ignore this feature for our purposes.

- Multiple strong conflicting drivers => short circuit
- Weak signals => circuit can't operate, unexpected results

❖ In Simulation

– Can detect x or z using special comparison operators

❖ In Reality

– Cannot detect x or z

– No actual 'x' – electrically just 0, 1, or z

– Except for some uninitialized signals, x is bad!

Number representation

- Representation: <size>'<base><number>
 - size => number of bits (regardless of base used)
 - base => base the given number is specified in
 - number => the actual value in the given base
- Can use different radix(base)
 - d or D : Decimal – default if no base specified!
 - h or H : Hexadecimal Hex
 - o or O : Octal
 - b or B : Binary
- Size defaults to at least 32.
 - You should specify the size explicitly!
 - Why create 32-bit register if you only need 5 bits?
 - May cause compilation errors on some compilers
- To be absolutely clear in your intent **it's usually best to explicitly specify the width and radix.**

Number	Decimal Equivalent	Actual Binary
4'd3	3	0011
8'ha	10	00001010
8'o26	22	00010110
5'b111	7	00111
8'b0101_1101	93	01011101
8'bx1101	-	xxxx1101
-8'd6	-6	11111010

Data types

- Verilog has two major data types:

Net and **Variable**(register)

- Nets

- Represent interconnects / physical connection from one point to other
- Primarily used only in dataflow and structural modeling
- Must be driven by a driver, such as a gate or continuous assignment statement
- Default value is high impedance
- Examples
 - `wire, wand, wor`
 - `tri, triand, trior`
 - `supply0, supply1`

- Signed vs Unsigned

- Net types and `reg` variables unsigned by default
- Have to declare them as signed if desired!
`reg signed [7:0] signedreg;`
`wire signed [3:0] signedwire;`

- Variable

- Represent interconnects / physical connection from one point to other
- Analogous to the concept of storage / holds some value
- Primarily used only in behavioral modeling
- There are various kinds
 - `reg` // stores a value, can be single bit or vector
 - `integer` // used in computations, is of 32 bits
 - `time` // used to see the simulation time
 - `real` // used to store real numbers, uses 64 bits
 - `realtime` // stores time as real numbers
- Need not necessarily result in flip-flop/ latch
- Default value is 'x'
- Cannot be driven by a gate

Operators

Operator Type	
Bitwise	~, &, , ^, ~^, ^~,
Logical	!, &&,
Unary/Reduction	&, ~&, ^, ~^, ^~, , ~
Relational	<, <=, >, >=
[In]Equality	==, !=, ===, !==
Conditional	?:
Arithmetic	+, -, ** (power) , *, /, %, >>, <<, >>>, <<<
Concatenation	{}, {{}}

Bitwise

~a	NOT
a & b	AND
a b	OR
a ^ b	XOR
a ~^ b a ^~ b	XNOR

Reduction

&a	AND
~&a	NAND
a	OR
~ a	NOR
^a	XOR
~^a ^~a	XNOR

Logical

!a	NOT
a && b	AND
a b	OR
a == b a != b	[in]equality returns x when x or z in bits. Else returns 0 or 1
a === b a !== b	case [in]equality returns 0 or 1 based on bit by bit comparison

Generate statement

- Simply replicates a given set of function for a specified number of time.
- Two types of generate statements available:
 - *For generate*
 - Variables used inside for generate loop known as '*genvar*'
 - Loop inside for generate should be labeled
 - *If generate*
 - Used for conditional use of hardware / logic
- Statement is concurrent in nature.

```
//Code for hierarchal design
module adder_bit_n #(parameter n = 8)
( output [n-1:0] sum,
  output carry_out,
  input [n-1:0] first, second,
  input carry_in );
  genvar j;
  wire [n:0] carry_wires;
  assign carry_wires[0] = carry_in;
  generate
    for (j=0; j < n; j = j+1)
      begin :series
        adder A(.A(first[j]),.Ci(carry_wires[j]),
               .B(second[j]), .Su(sum[j]),
               Co(carry_wires[j+1]));
      end
  endgenerate
  assign carry_out = carry_wires[n];
endmodule
```


Behavioral Modeling

- Most advanced coding style which is flexible, high-level and closest to software programming languages.
- Behavior: Actions a circuit is supposed to perform when it is active.
- Present day problems are quite complex and so are the solutions. Functionality required is known but not hardware.
- Behavior of system can be very easily explained in higher level abstraction.
- Represents both concurrent and sequential behaviour of hardware
- Repetitive task can be expressed only once and then called many number of times
- Uses **procedural blocks** which are of two types:
 - *initial*
 - *always*
- Can have more than one procedural blocks. All procedural blocks work in parallel / concurrent in nature. Each procedural block contain set of statements which execute sequentially.

Ports and Datatypes

We can add the *reg* keyword to *output* or *inout* ports (we wouldn't be assigning values to *input* ports!), or we can declare nets using *reg* instead of *wire*.

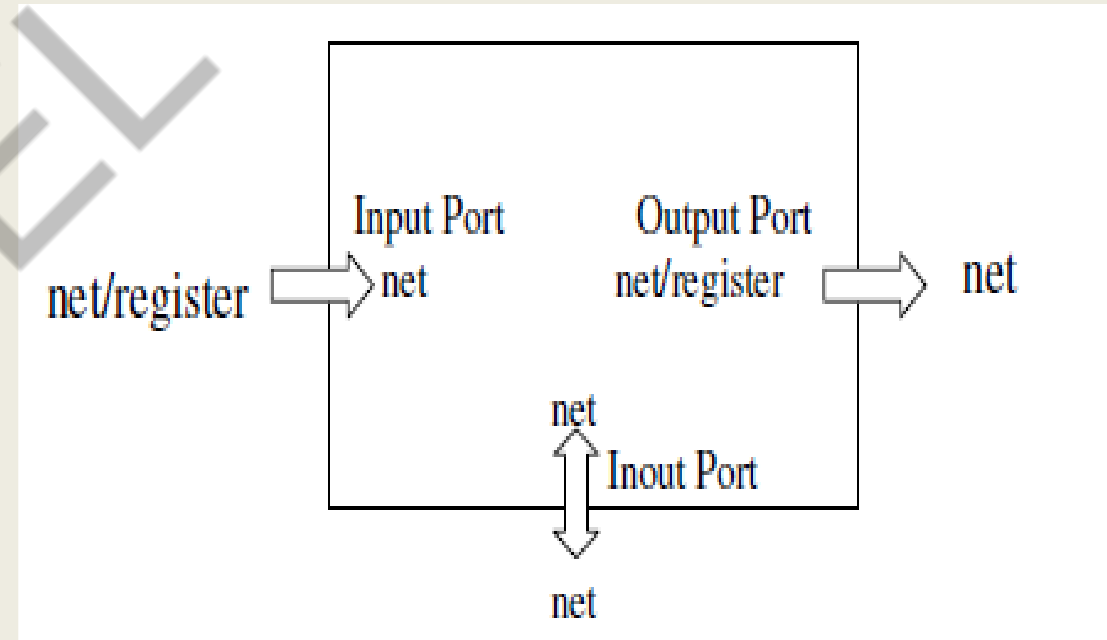We've been using *wire* declarations when naming nets (ports are declared as wires by default). However nets appearing on the LHS of assignment statements inside of *always* blocks **must** be declared as type *reg*.



Procedural blocks

Initial

- Used primarily to initialize variables and in testbenches.
- Terminates when control reaches the end.
- Will not synthesize into hardware.
- More than one statement in a block needs to be grouped with '*begin*' & '*end*'
- Multiple initial blocks start execution in parallel at time 0 and end independent of other blocks.
- Will not have sensitivity list

Always

- Used to describe the functionality of a system
- Restarts when control reaches the end.
- Will synthesize into hardware as defined by statements written inside the block.
- More than one statement in a block needs to be grouped with '*begin*' & '*end*'
- Multiple 'always' blocks execute in parallel
- May have a sensitivity list

Procedural block : Examples

```
initial  
begin  
  a = 3'b0;  
  #10 clr = 1'b0;  
  #21 clr = 1'b1;  
end
```

```
initial  
begin: test_loop  
  integer i;  
  for (i=0; i<=15; i=i+1;  
    #5 test_in = i;  
end
```

```
module comparator(  
  output reg dgv, dlv, dev,  
  input [4:0] data, value);  
  always@(data, value)  
  begin  
    dgv = (data > value);  
    dlv = (data < value);  
    dev = (data == value);  
  end  
endmodule
```

Conditional statement

- Statements written inside procedural blocks are known as **procedural assignment statements**.
- There are two sub-classes known as
 - conditional assignment statements
 - if-else, case
 - loop statements
 - for, while, forever, repeat
- Some of these statements synthesize while others do not.
- Conditional statements are behavioral equivalent of the conditional operator.
 - These can be nested as many times as needed
 - When written properly will infer a multiplexer or mux like structure

```
// 4-to-1 multiplexer
module mux4(
    input a,b,c,d, input [1:0] sel, output
    reg z,zbar);
    always @(*)
    begin
        if (sel == 2'b00) z = a;
        else if (sel == 2'b01) z = b;
        else if (sel == 2'b10) z = c;
        else if (sel == 2'b11) z = d;
        else z = 1'bx;
    /* when sel is X or Z , statement order
    matters inside always blocks so the
    following assignment happens *after*
    the if statement has been evaluated*/
        zbar = ~z;
    end
endmodule
```

Case statement


- Chains of **if-then-else** statements aren't the best way to indicate the intent to provide an alternative action for every possible control value.
- *case* looks for an exact bit-by-bit match of the value of the case expression (e.g., sel) against each case item, working through the items in the specified order. *casex/casez* statements treat X/Z values in the selectors as don't cares when doing the matching that determines which clause will be executed.

```
// 4-to-1 multiplexer
module mux4(
    input a,b,c,d, input [1:0] sel, output reg
    z,zbar);
    always @(*)
    begin
        case (sel)
            2'b00: z = a;
            2'b01: z = b;
            2'b10: z = c;
            2'b11: z = d;
            default: z = 1'bx; // in case sel is X or Z
        endcase
        zbar = ~z;
    end
endmodule
```

Sensitivity list and Timing control

- An always block may or may not have any sensitivity list
- Sensitivity list controls when the block will be executed
- An always block without sensitivity list and no timing control statements will act like an infinite loop.
- Example
 - *always*
 - *always* @(*) → blocks are evaluated whenever any value used inside changes.
 - Equivalently we could have written *always* @(a, b, c, d, sel) *begin ... end*
- Timing control will stop/ delay the simulator from executing the remaining piece of code until some condition is true
- There are 2 kinds of timing controls
 - Delay Based (Postpones the simulation for some time)
 - Inter assignment delay,
 - Intra assignment delay
 - Event Based (Suspends the simulation for some time)
 - *always* @(data, value)
 - *wait*(enable)

Test bench structure

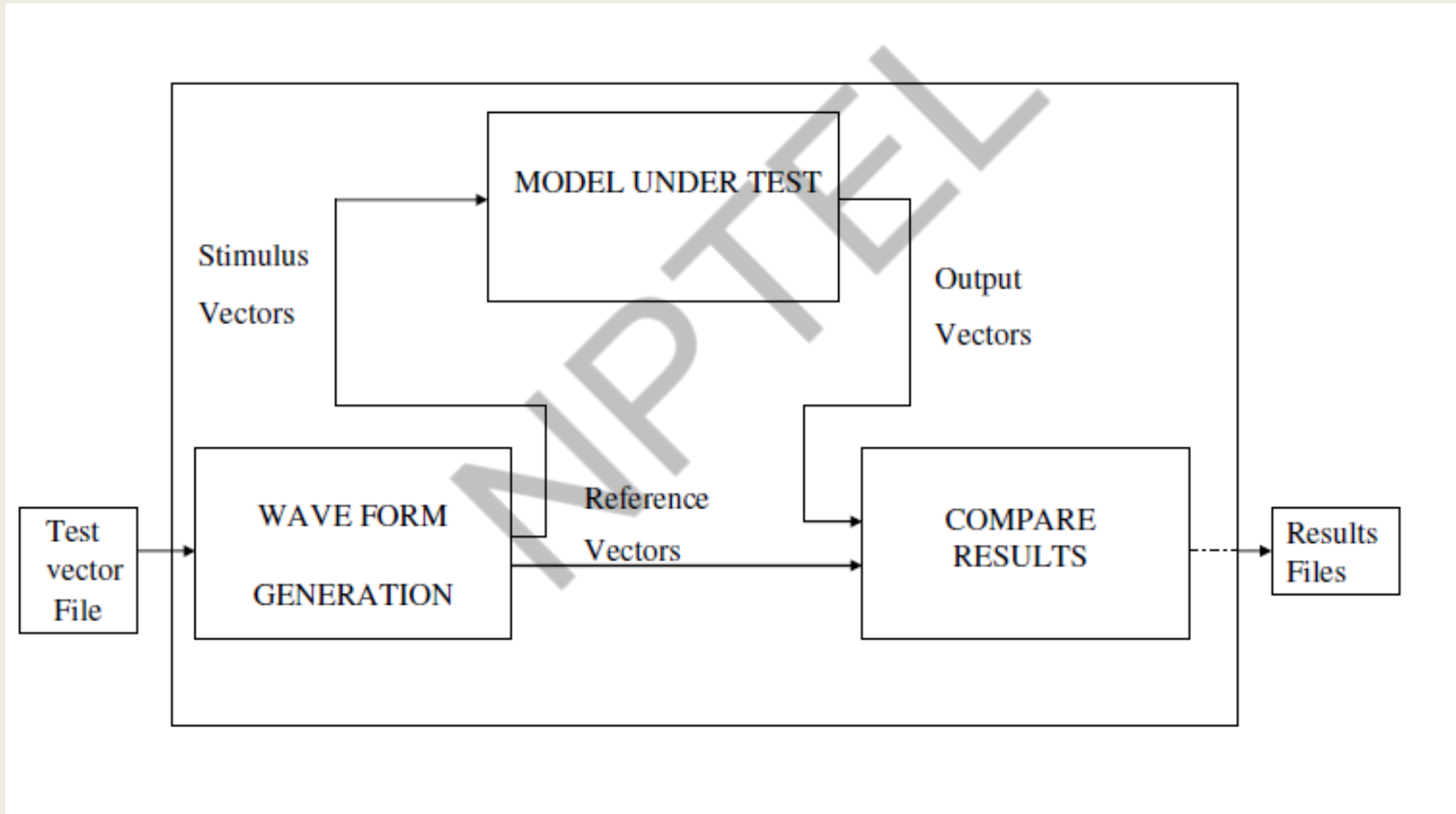

Components of test bench

- The simplest test benches are those that apply some sequence of inputs to the circuit being tested so that its operation can be observed in simulation.
- Waveforms are typically used to represent the values of signals in the design at various points in time
- A test bench must consist of a component declaration corresponding to the unit under test(UUT), and a description of the input stimulus being applied to the UUT.
- A test bench is a top level module without inputs and outputs
 - Data type declaration
 - Declare storage elements to store the test patterns
 - Module instantiation
 - Instantiate pre-defined modules in current scope
 - Applying stimulus
 - Describe stimulus by behavior modeling
 - Stimuli are given by variables of data type register
 - Display results
 - Response is captured by variables of data type net
 - By text output, graphic output, or waveform display tools
- Three kinds of testbenches are in use
 - One which only supplies the stimuli
 - One which not only supplies stimuli but also captures the result
 - One which supplies stimuli, captures result and also carries out timing check

Test bench example

```
module full_adder
( input a, b, cin,
  output reg sum, cout);
always @(a or b or cin)
begin
sum = a ^ b ^ cin;
cout = (a & b) | (a & cin) | (b & cin);
end
endmodule
```

```
module full_adder_4bit
( input [3:0] a, b,
  input cin,
  output [3:0] sum,
  output cout),
wire c1, c2, c3;
// instantiate 1-bit adders
full_adder FA0(a[0],b[0], cin, sum[0], c1);
full_adder FA1(a[1],b[1], c1, sum[1], c2);
full_adder FA2(a[2],b[2], c2, sum[2], c3);
full_adder FA3(a[3],b[3], c3, sum[3],
cout);
endmodule
```

```
module test_adder;
reg [3:0] a, b;
reg cin;
wire [3:0] sum;
wire cout;
full_adder_4bit dut(a, b, cin,sum, cout);
initial
begin
a = 4'b0000;
b = 4'b0000;
cin = 1'b0;
#50;
a = 4'b0101;
b = 4'b1010;
// sum = 1111, cout = 0
#50;
a = 4'b1111;
b = 4'b0001;
// sum = 0000, cout = 1
#50;
a = 4'b0000;
b = 4'b1111;
cin = 1'b1;
// sum = 0000, cout = 1
#50;
a = 4'b0110;
b = 4'b0001;
// sum = 1000, cout = 0
end // initial begin
endmodule // test_adder
```

Compiler directives

- Macro definitions: ``define`
- Conditional compilation: ``ifdef, ...`
- Include other source files: ``include`
- Control simulation time units: ``timescale`
- No implicit net declarations: ``default_nettype none`

References

- [Slide source1](#)
- [Slide source2](#)
- [IEEE Verilog 2001 Standard](#)
- [Comparision of HDLs](#)